 


FINAL PROJECT REPORT

14TH JULY, 2023

DESIGN AND IMPLEMENTATION 8 - BIT ARITHMETIC LOGIC UNIT USING CMOS

USING CADENCE VIRTUOSO



Prepared By:

21BEC1662 - RAGHUL G

21BEC1692 - OVISHREE S

21BEC1655 - NIRANJANA D

21BEC1625 - RAGUL D

This project contain an Arithmetic & Logic Unit (ALU) using logic gates.


This ALU will perform 5 different operations:

- LOGIC NOT
- LOGIC AND
- LOGIC OR
- ARITHMETIC ADDITION
- ARITHMETIC SUBTRACTION


INSTRUCTION TABLE OF ALU

FO	F1	F2	OPERATIONS
0	0	0	NOT
0	0	1	AND
0	1	0	OR
0	1	1	FULL ADDER
1	0	0	FULL SUBTRACTOR

1 BIT ALU CIRCUIT

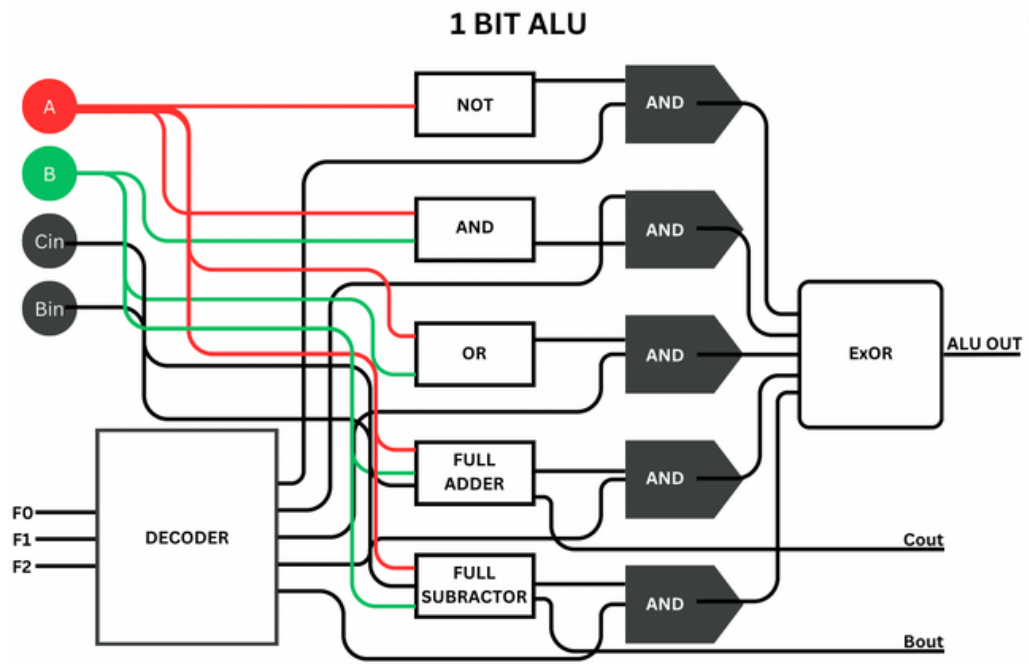


1 BIT ALU SYMBOL

 


8 BIT ALU SYMBOL


8 BIT ALU

 


DECODER CIRCUIT

 


DECODER SYMBOL

 


NOT GATE CIRCUIT

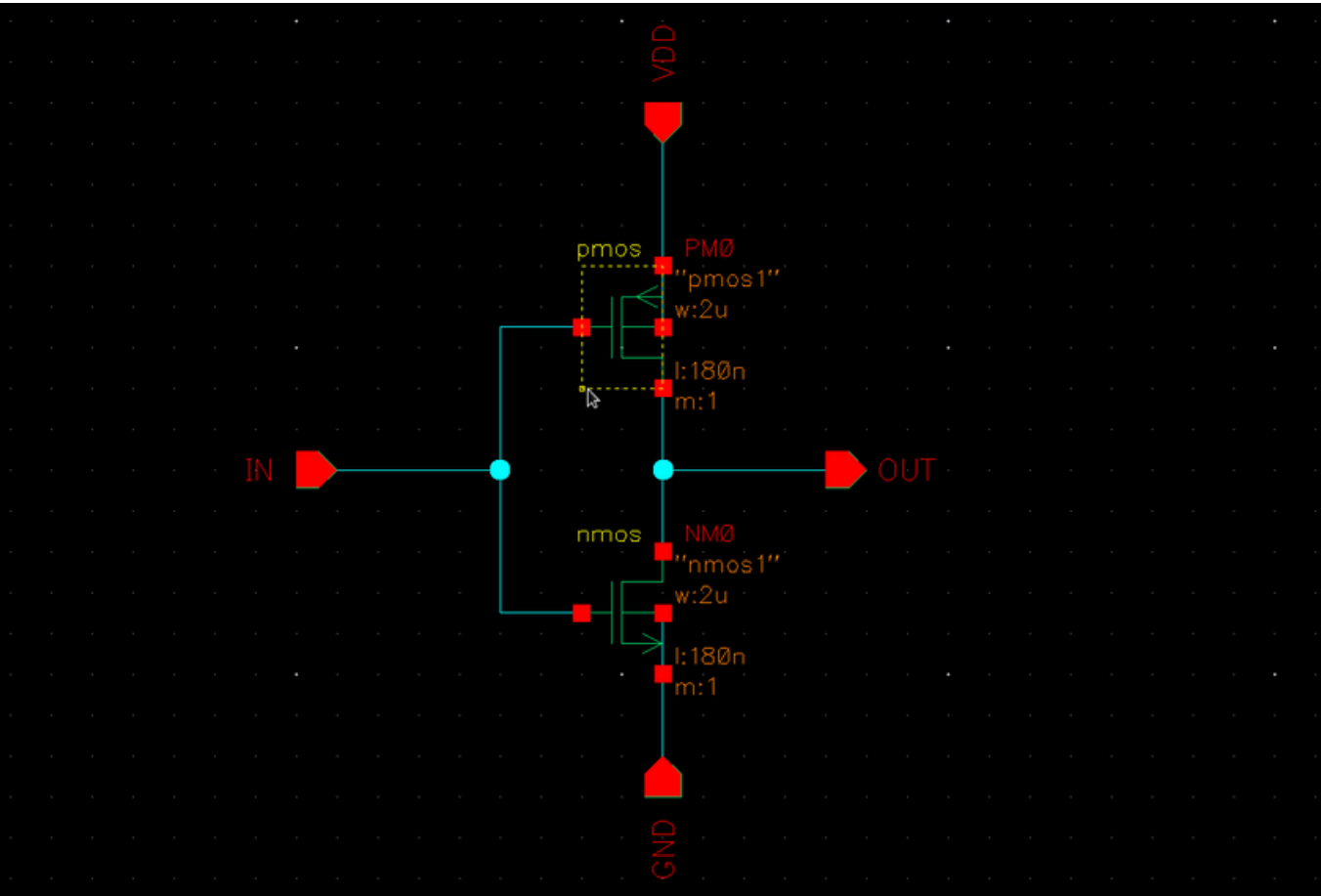


NOT GATE SYMBOL

 


AND GATE CIRCUIT

 


AND GATE SYMBOL

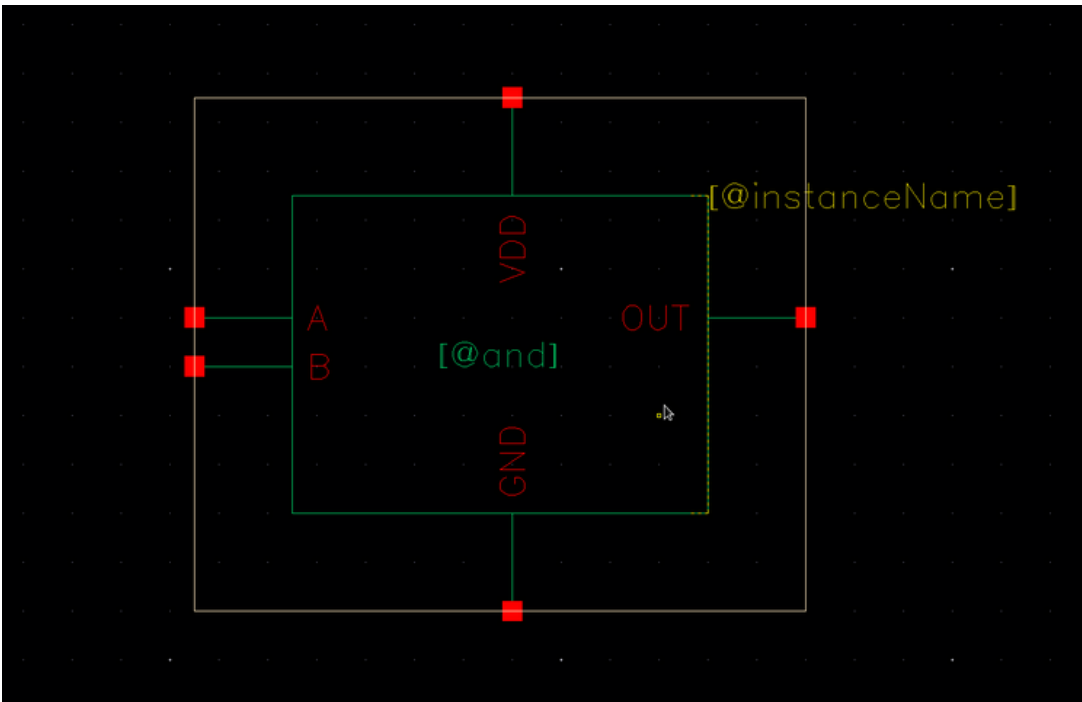


OR GATE CIRCUIT

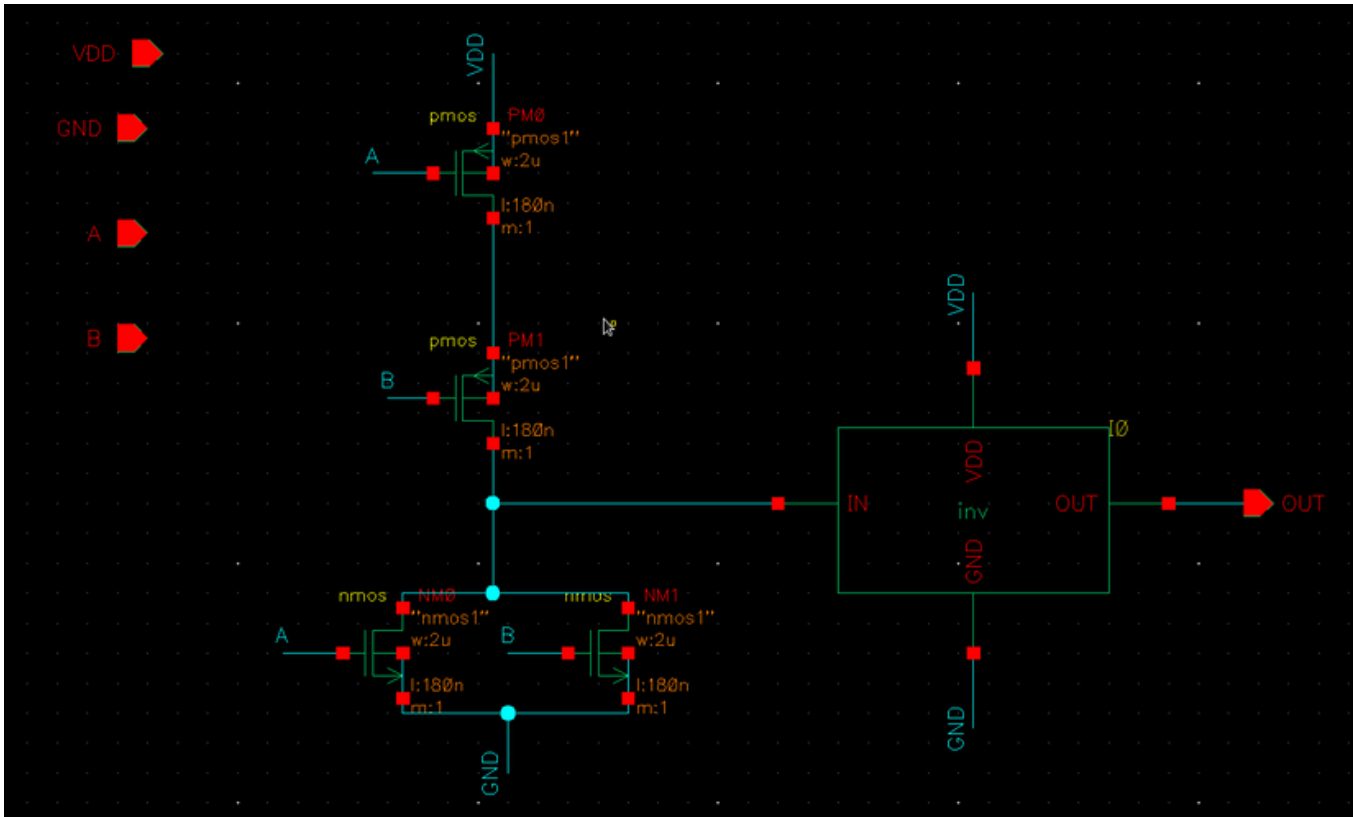


OR GATE SYMBOL

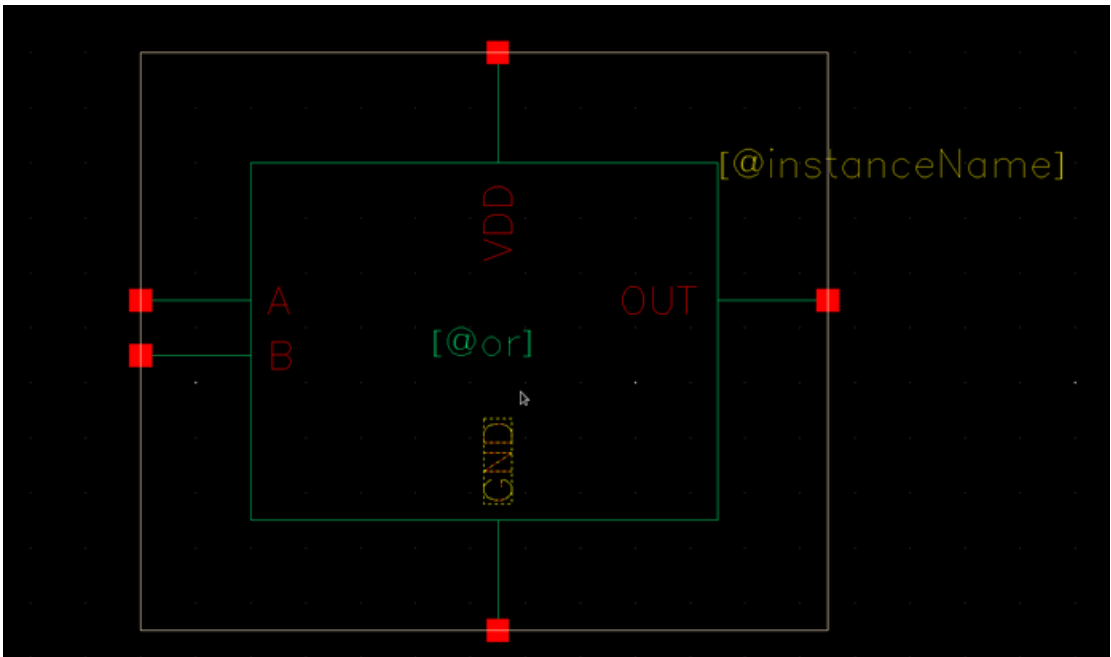


FULL ADDER CIRCUIT

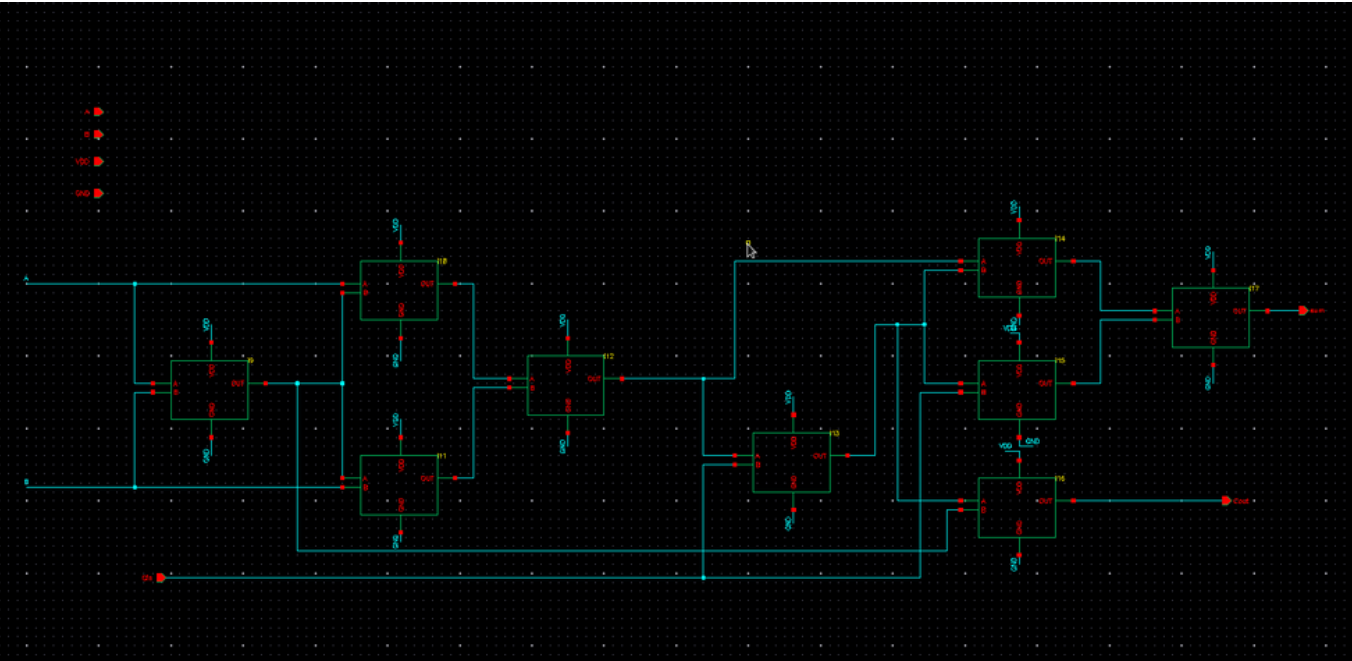


FULL ADDER SYMBOL

 


FULL SUBTRACTOR CIRCUIT

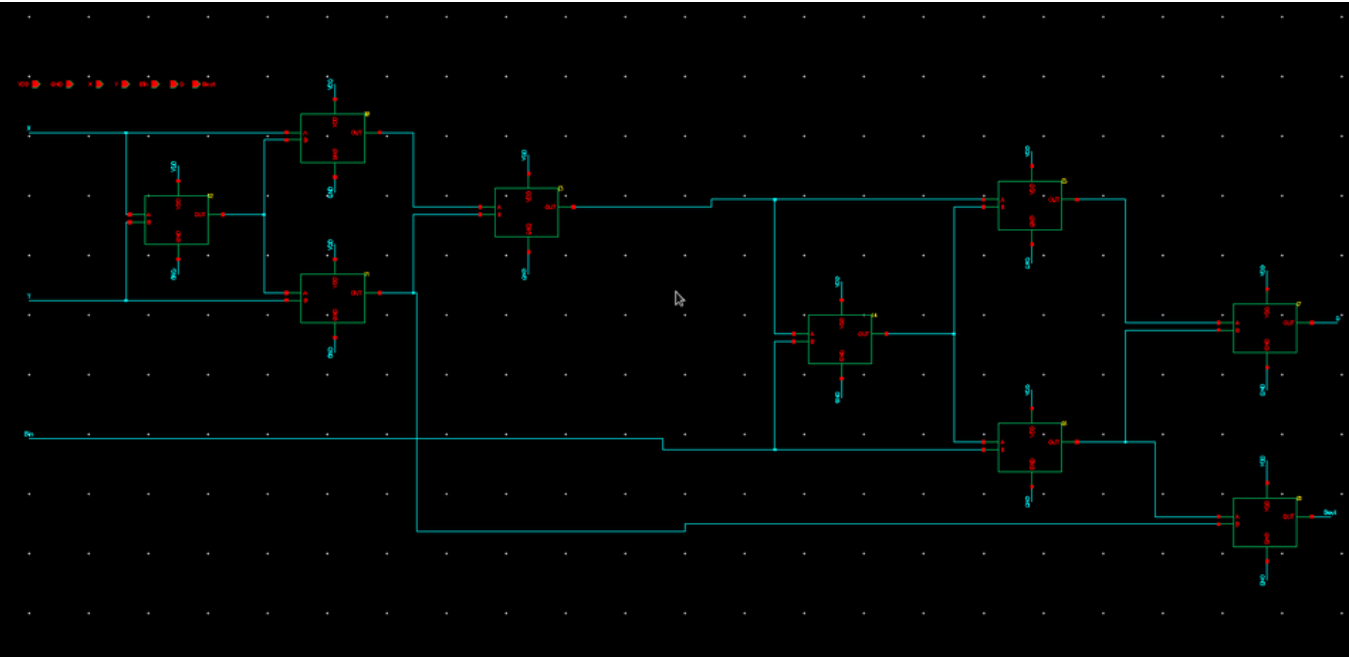


FULL SUBTRACTOR SYMBOL

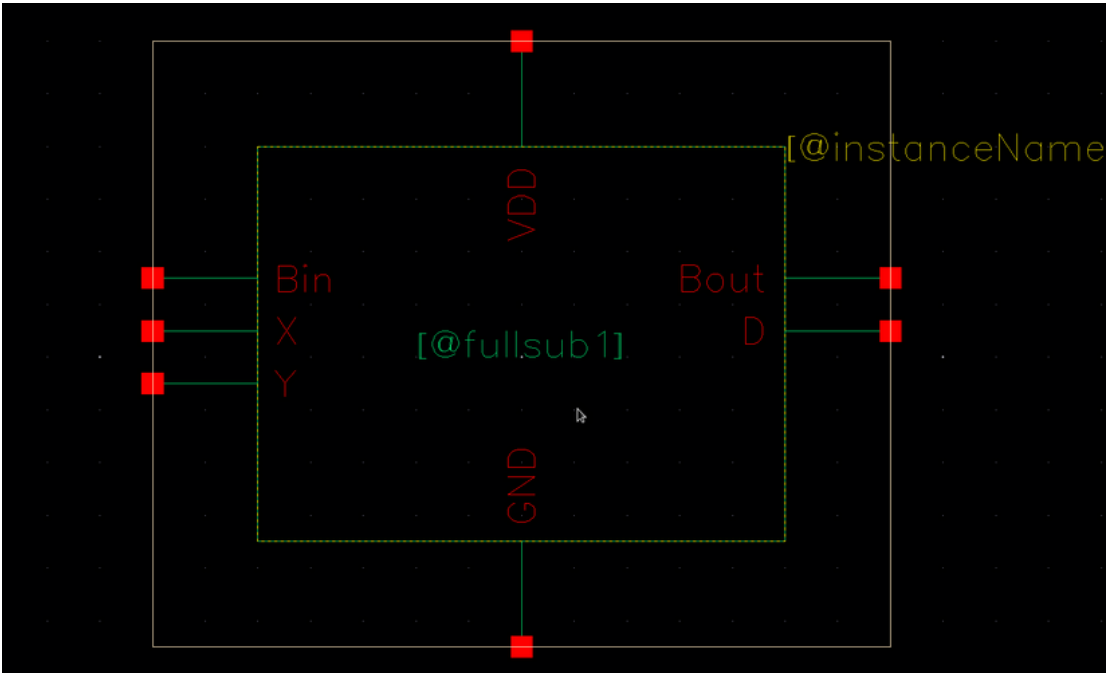


1 BIT ALU CIRCUIT

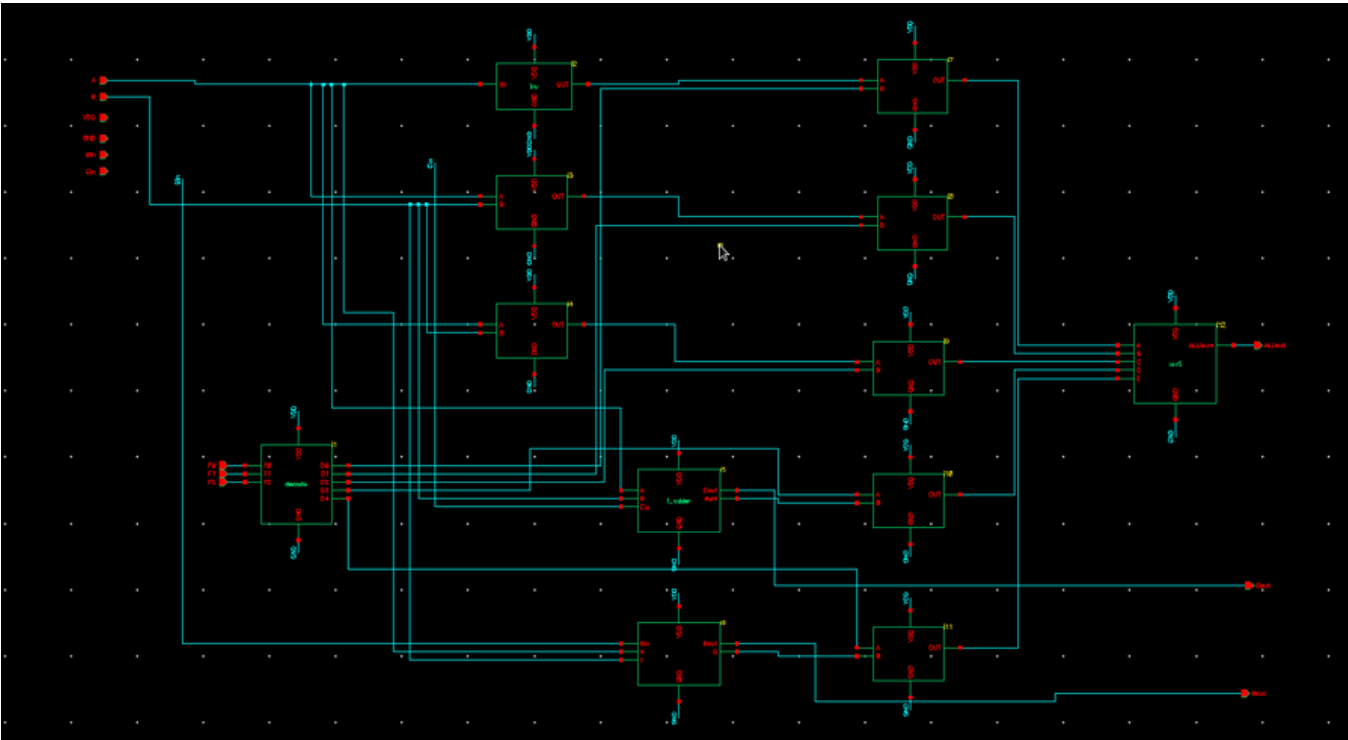

1 BIT ALU SYMBOL

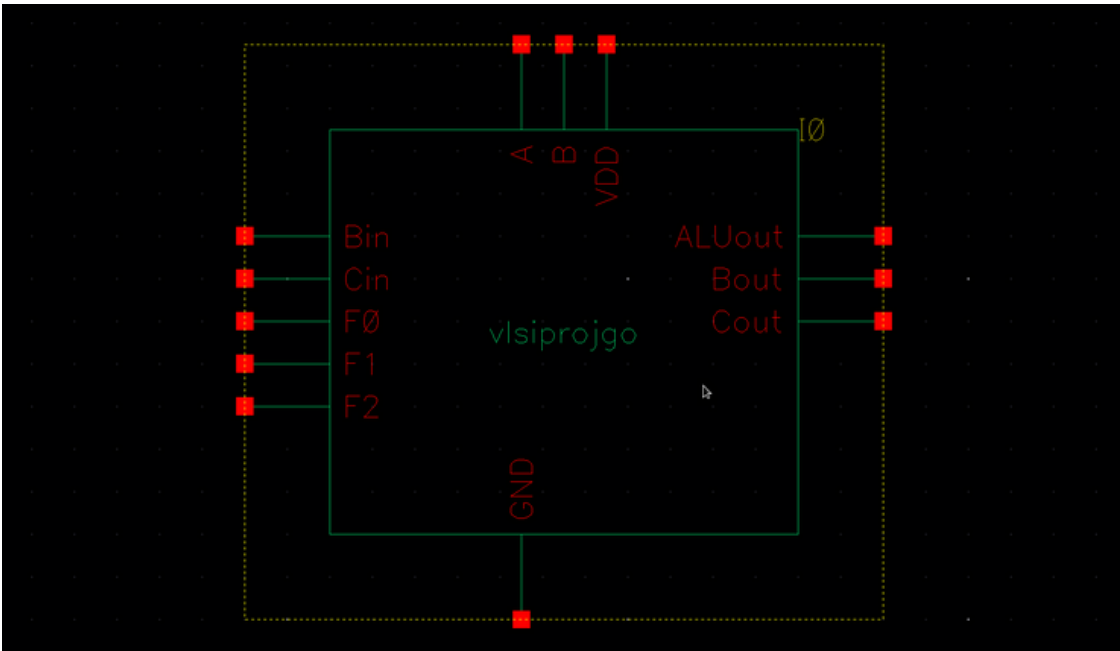

8 - BIT ALU

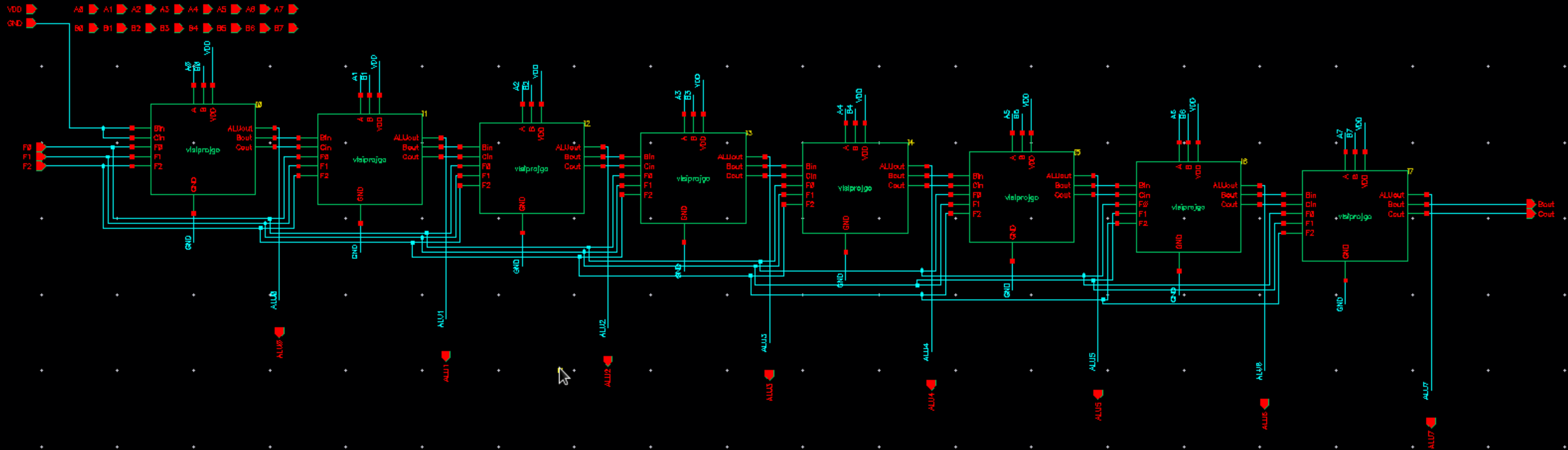


RESULT

COMBINATION 1


INPUTS		ALU OPERATIONS				
AO	BO	NOT	AND	OR	FA	FS
0	0	1	0	0	0	0
1	1	0	1	1	0	0
1	0	0	0	1	0	1
0	1	1	0	1	0	1
1	0	0	0	1	0	0
0	1	1	0	1	0	1
0	0	1	0	0	1	1
1	1	0	1	1	0	1

Cout = 1
Bout = 1


NOT

 


AND

 


OR

 

FULL ADDER

 

FULL SUBTRACTOR

 


COMBINATION 2


INPUTS		ALU OPERATIONS				
AO	BO	NOT	AND	OR	F A	F S
1	0	0	0	1	1	1
0	1	1	0	1	1	1
0	0	1	0	0	0	1
1	1	0	1	1	0	1
0	0	1	0	0	1	1
1	1	0	1	1	0	1
1	0	0	0	1	0	0
0	1	1	0	1	0	1

Cout = 1
Bout = 1


NOT

 


AND

 


OR

 

FULL ADDER

 

FULL SUBTRACTOR

 

RESULT:

We have implemented 8 Bit ALU which contains logical NOT, AND, OR and Arithmetic ADDER and SUBTRACTOR using cadence.

We can infer that both Theoretical and Graphical values are same.

THANK YOU